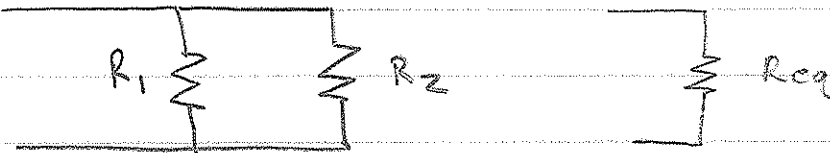


ME 104 HOMEWORK #1 SOLUTIONS

2.3



$$R_1 = \text{Brown Black Red Gold} = 10 \times 10^2 \pm 5\% = 1 \text{ k}\Omega \pm 5\%$$

$$R_2 = \text{Red Green Brown Gold} = 25 \times 10^1 \pm 5\% = 250 \pm 5\%$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} \quad (\text{NOMINAL}) \quad R_{eq} = 200 \Omega$$

$$\frac{1}{R_{eq-tol}} = \frac{1}{R_1(0.95)} + \frac{1}{R_2(0.95)} \quad R_{eq-tol} = 190 \Omega$$

$$\frac{1}{R_{eq+tol}} = \frac{1}{R_1(1.05)} + \frac{1}{R_2(1.05)} \quad R_{eq+tol} = 210 \Omega$$


SO PICK

$$R = 200 \Omega$$

$$tol = 5\%$$

COLOR: a = Red b = BLACK c = BROWN tol = GOLD

2.8

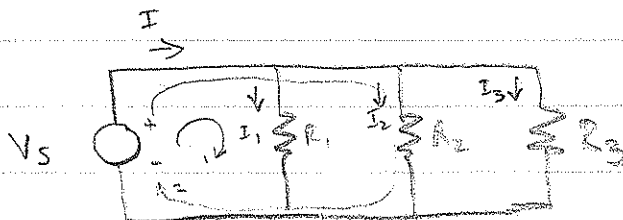

$$\text{KCL} \quad I = I_1 + I_2 + I_3$$

$$\text{KVL} \quad \textcircled{1} \quad V_s = I_1 R_1$$

$$V_s = I R_{eq}$$

$$\textcircled{2} \quad V_s = I_2 R_2$$

$$V_s = I R_3$$

$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} = \frac{R_1 R_2 R_3}{R_1 R_2 + R_2 R_3 + R_1 R_3}$$

- CONT. -

$$\text{So, } I_1 = \frac{V_s}{R_1} = \frac{I R_{eq}}{R_1} = \frac{R_{eq}}{R_1} I$$


$$I_1 = \left(\frac{R_2 R_3}{R_1 R_2 + R_2 R_3 + R_1 R_3} \right) I$$

LIKEWISE

$$I_2 = \left(\frac{R_1 R_3}{R_1 R_2 + R_2 R_3 + R_1 R_3} \right) I$$

$$I_3 = \left(\frac{R_1 R_2}{R_1 R_2 + R_2 R_3 + R_1 R_3} \right) I \quad \square$$

2.10

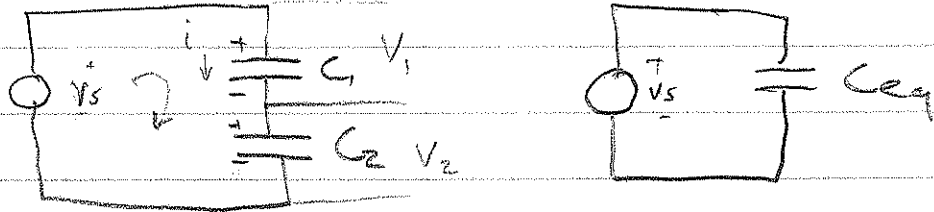

KVL $V_s - V_1 - V_2 = 0$ $\frac{dV_s}{dt} - \frac{dV_1}{dt} - \frac{dV_2}{dt} = 0$

$$i = \frac{dV_s}{dt} C_{eq}$$


$$i = \frac{dV_1}{dt} C_1$$

$$i = \frac{dV_2}{dt} C_2$$

$$\Rightarrow \frac{i}{C_{eq}} = \frac{i}{C_1} + \frac{i}{C_2} \Rightarrow \frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$$

$$C_{eq} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2}} = \frac{C_1}{1 + \frac{C_1}{C_2}} = \frac{C_1 C_2}{C_1 + C_2} \quad \square$$

2.27

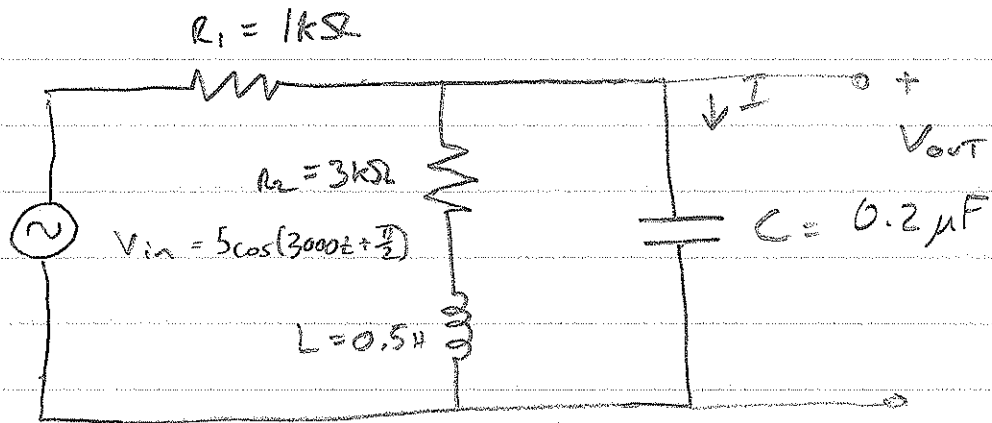

FROM EXAMPLE 2.7


$$I(t) = 2.22 \angle 159.8^\circ \text{ mA}$$

AND RECALL: $Z_C = \frac{1}{j\omega C} = \frac{-j}{\omega C} = \frac{1}{\omega C} \angle -90^\circ$


$$\begin{aligned} \text{SO } \hat{V}_{out} &= \hat{I} Z_C = (2.22 \times 10^{-3} \angle 159.8^\circ) \left(\frac{1}{3000 \cdot 0.2 \mu\text{F}} \angle -90^\circ \right) \\ &= (2.22 \times 10^{-3} \angle 159.8^\circ) \left(\frac{1}{\underset{\substack{\uparrow \\ 3 \times 10^3}}{3000} \cdot \underset{\substack{\uparrow \\ 0.2 \times 10^{-6}}}{0.2 \mu\text{F}}} \angle -90^\circ \right) \\ &= (2.22 \times 10^{-3} \angle 159.8^\circ) (1.66 \times 10^3 \angle -90^\circ) \\ &= 3.69 \angle 69.8^\circ = 3.69 \angle 1.22 \text{ rad} \end{aligned}$$

SO $V_{out}(t) = 3.69 \cos(3000t + 1.22) \text{ V}$

2.29

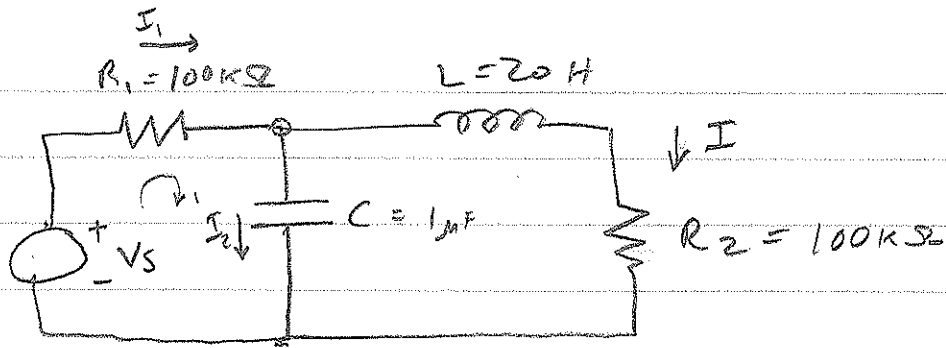FIND $I(t)$ a) $V_s = 5V$ DC

AT DC, THE CIRCUIT BECOMES

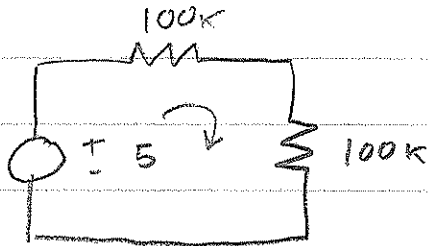

$$R_{eq} = R_1 + R_2 = 200 \text{ k}\Omega$$

$$I = \frac{V}{R_{eq}} = 0.025 \text{ mA}$$

b) $V_s = 5 \cos(\pi t) V$

$$\hat{V}_s = 5$$

KVL

$$\text{Loop 1: } \hat{V}_s = \hat{I}_1 R_1 + \hat{I}_2 Z_C$$

$$\text{Outer Loop: } \hat{V}_s = \hat{I}_1 R_1 + \hat{I}(Z_L + R_2)$$

KCL

$$\text{TOP NODE: } \hat{I}_1 = \hat{I}_2 + \hat{I}$$

$$\underbrace{\begin{bmatrix} R_1 & Z_C & 0 \\ R_1 & 0 & (Z_L + R_2) \\ 1 & -1 & -1 \end{bmatrix}}_A \underbrace{\begin{bmatrix} \hat{I}_1 \\ \hat{I}_2 \\ \hat{I} \end{bmatrix}}_X = \underbrace{\begin{bmatrix} \hat{V}_s \\ \hat{V}_s \\ 0 \end{bmatrix}}_b$$

— CONT —

4/6

$$x = A^{-1} b$$

$$\Rightarrow \hat{I} = 2.4398 \times 10^{-5} - 3.8405 \times 10^{-6} j$$

$$= 0.0247 \text{ mA} \angle -0.156 \text{ rad} \quad \text{or } \angle -8.9^\circ$$

$$\text{so } \boxed{I(t) = 0.0247 \cos(\pi t - 0.156)}$$

□

5. $e^x = \sum_{n=0}^{\infty} \frac{x^n}{n!}$; $\sin x = \sum_{n=0}^{\infty} \frac{(-1)^n}{(2n+1)!} x^{2n+1}$; $\cos x = \sum_{n=0}^{\infty} \frac{(-1)^n}{(2n)!} x^{2n}$

EXPAND TO EVEN & ODD, AND SEPARATE

$$e^x = \sum_{n=0}^{\infty} \frac{x^n}{n!} = \sum_{n=0}^{\infty} \frac{x^{2n}}{(2n)!} + \sum_{n=0}^{\infty} \frac{x^{2n+1}}{(2n+1)!} = \sum_{n=0}^{\infty} \frac{x^{2n}}{(2n)!} + \sum_{n=0}^{\infty} \frac{x^{2n+1}}{(2n+1)!}$$

NOW, SUBSTITUTE $x = j\theta$

$$e^{j\theta} = \sum_{n=0}^{\infty} \frac{(j\theta)^{2n}}{(2n)!} + \sum_{n=0}^{\infty} \frac{(j\theta)^{2n+1}}{(2n+1)!} = \sum_{n=0}^{\infty} \frac{j^{2n}}{(2n)!} \theta^{2n} + \sum_{n=0}^{\infty} \frac{j^{2n+1}}{(2n+1)!} \theta^{2n+1}$$

AND RECALL $j^{2n} = (-1)^n \quad \forall n \in \mathbb{Z}$

$$j^{2n+1} = j(-1)^n \quad \forall n \in \mathbb{Z}$$

$$\text{so } e^{j\theta} = \underbrace{\sum_{n=0}^{\infty} \frac{(-1)^n}{(2n)!} \theta^{2n}}_{\cos \theta} + j \underbrace{\sum_{n=0}^{\infty} \frac{(-1)^n}{(2n+1)!} \theta^{2n+1}}_{\sin \theta}$$

$$e^{j\theta} = \cos \theta + j \cdot \sin \theta$$

□

6.

$$r e^{j\theta} = 1 - 2j$$

$$r = \sqrt{1^2 + 2^2} = \sqrt{5} = 2.24$$

$$\theta = \text{atan2}(-2, 1) = -1.11 \text{ rad} = -63.4^\circ$$

$$= 5.12 \text{ rad} = 296.5^\circ$$

7.

$$(1+2j)^{-1} = x + jy$$

$$1 = (1+2j)(x+jy)$$

$$1 = x + yj + 2xj - 2y$$

$$1 = x - 2y + (2x + y)j$$

$$\text{Re}\{1\} = \text{Re}\{x - 2y + (2x + y)j\}$$

$$\Rightarrow 1 = x - 2y$$

$$\text{Im}\{1\} = \text{Im}\{x - 2y + (2x + y)j\}$$

$$\Rightarrow 0 = 2x + y$$

SOLVE

$$\underbrace{\begin{bmatrix} 1 & -2 \\ 2 & 1 \end{bmatrix}}_A \underbrace{\begin{bmatrix} x \\ y \end{bmatrix}}_x = \underbrace{\begin{bmatrix} 1 \\ 0 \end{bmatrix}}_b$$

$$A^{-1}b = \begin{bmatrix} x \\ y \end{bmatrix} = \begin{bmatrix} 1/5 \\ -2/5 \end{bmatrix}$$

$$\text{So } (1+2j)^{-1} = 1/5 - 2/5 j$$