

ME104 Midterm I  
1 hour and 10 minutes  
Closed book & notes, no calculators.

Problem 0. What is your name?

Solutions.

Problem 1. Compute the magnitude and phase of  $\frac{1+j}{1-j}$ .

$$\frac{1+j}{1-j} \left( \frac{1+j}{1+j} \right) = \frac{2j}{2} = j$$

$$\text{Magnitude} = 1$$

$$\text{Phase} = +90^\circ$$

$$= 1 \angle 90^\circ$$

Problem 2. Find the phasor representing

a)  $\cos(\omega t)$

b)  $4 \sin(3t + \frac{\pi}{4})$

$$\text{a) } \cos \omega t = 1 \angle 0^\circ$$

$$\begin{aligned} \text{b) } 4 \sin(3t + \pi/4) &= 4 \cos\left(\frac{\pi}{2} - 3t - \frac{\pi}{4}\right) \\ &= 4 \cos\left(\frac{\pi}{4} - 3t\right) = 4 \cos\left(3t - \pi/4\right) \\ &= 4 \angle -\pi/4 = 4 \angle -45^\circ = 4 \angle 45^\circ \end{aligned}$$


Problem 3. Find the sinusoid represented by the phasor  $-j$ .

$$-j = -1 \angle 90^\circ$$

$$= -1 \cos(\omega t + 90^\circ)$$


$$= \sin \omega t$$

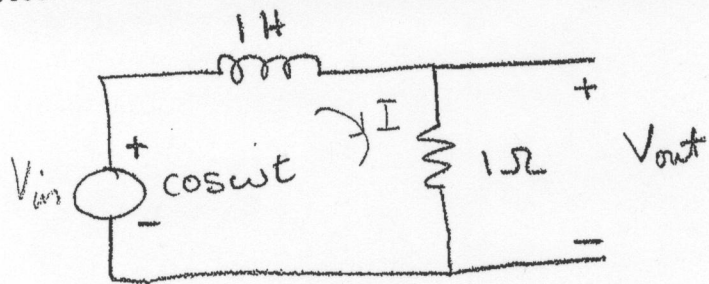Problem 4. Find sinusoidal steady state of  $V_{out}$  in the circuit below.



Step #1 Convert to phasors

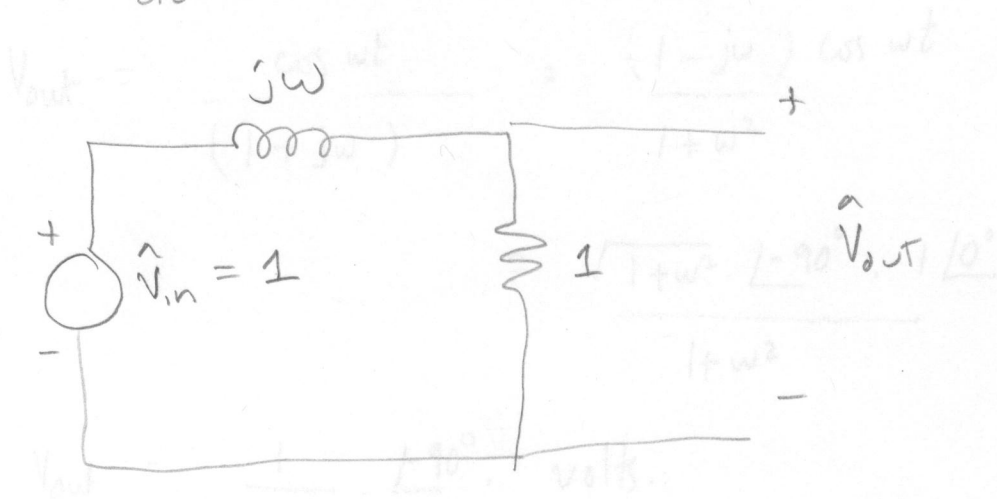Step #2  $\frac{d}{dt} \rightarrow j\omega$  (insert complex impedances)



Step #3 Solve

using impedance divider formula


$$\hat{V}_{out} = \frac{1}{1 + j\omega} \cdot \hat{V}_{in} = \frac{1}{1 + j\omega}$$

Step #4 convert to sinusoids

$$V_{out}(t) = |\hat{V}_{out}| \cos(\omega t + \angle \hat{V}_{out})$$


$$= \frac{1}{\sqrt{1 + \omega^2}} \cos(\omega t - \arctan(\omega))$$

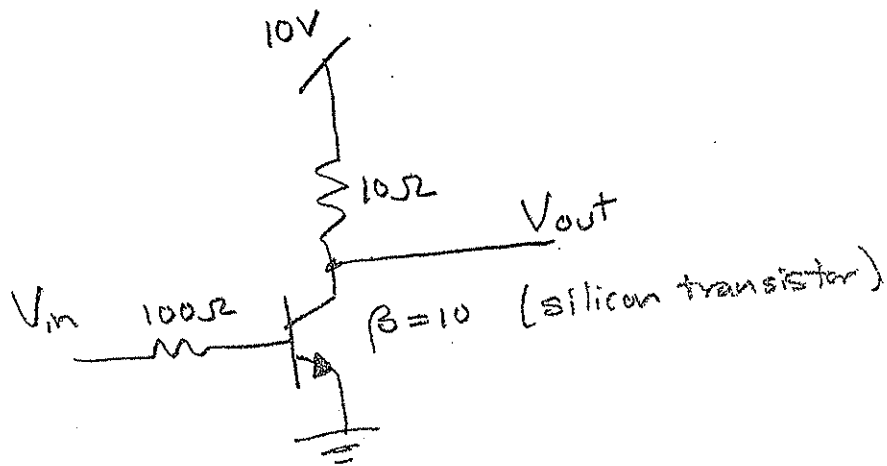Problem 5. Plot  $V_{out}$  versus  $V_{in}$  for the circuit below.



$$V_{in} = I_b(100) + V_{be} = 0.7 + 100I_b$$
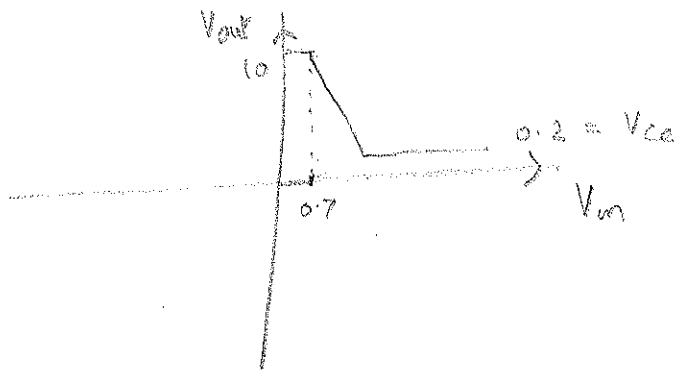
$$V_{out} = 10 - \beta I_b(10) = 10 - 100I_b$$



when  $V_{in} > V_{be} = 0.7$ ,  
transistor conducts  
 $\therefore V_{out} = V_{ce} = 0.2$

when  $V_{in} < V_{be}$ ,  $T_x$  is in  
cut off.

$$\therefore V_{out} = 10V$$

6. Show that the mechanical impedance of a mass is  $-j\omega m$ .



We know for mass  $m$ ,


$$f = m \cdot \frac{d^2x}{dt^2}$$

Substitute  $\frac{d}{dt} \rightarrow j\omega$

$$\therefore f = m (j\omega)^2 \cdot x = -m\omega^2 x$$

$$\text{Impedance} = \frac{f}{x} = \underline{-m\omega^2}$$

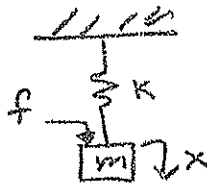7. What is the mechanical impedance  $\frac{f}{x}$  for the system below.



$$f = m \cdot \frac{d^2x}{dt^2} + Kx$$

$$f = m (j\omega)^2 x + Kx$$

$$= -m\omega^2 x + Kx$$

$$\therefore \frac{f}{x} = \underline{-m\omega^2 + K}$$